
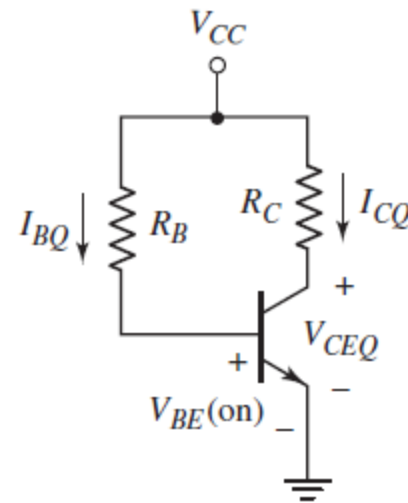


Biasing BJT Circuits

Dr. E.Papanasam
papanasam.e@vit.ac.in
AP Senior
School of Electronics
VIT Chennai

Single Base Resistor Biasing


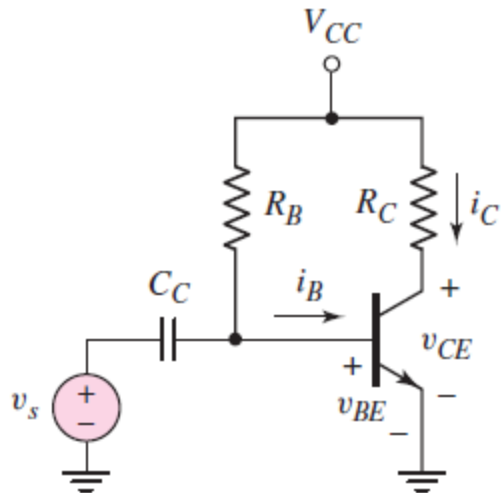
- Common-emitter circuit with a single bias resistor in the base and dc equivalent circuit



- Quiescent base current is established through the resistor R_B
- The **coupling capacitor** C_C acts as an open circuit to dc
 - Isolating the signal source from the dc base current
- Q-point** values are indicated by the additional subscript **Q**

Design Example

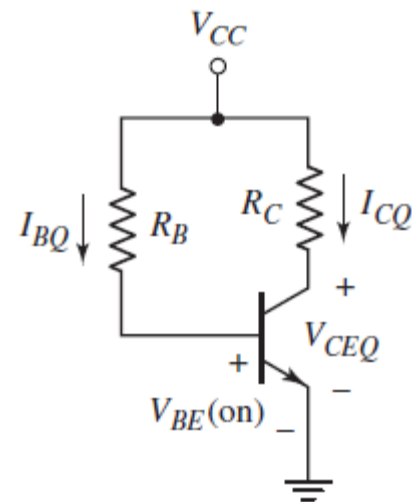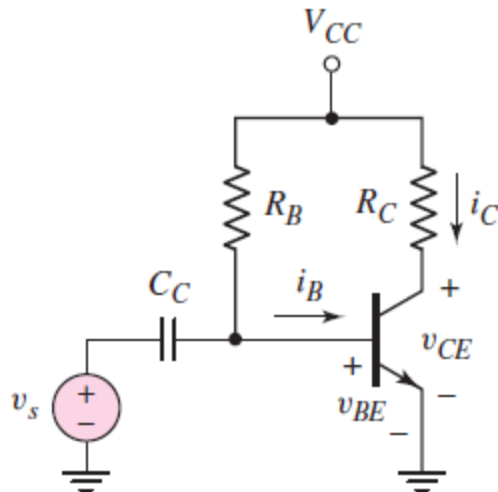- **Design** a circuit with a single-base resistor to meet a set of specifications.
- Specifications: The circuit is to be biased with $V_{CC} = +12\text{ V}$. The transistor quiescent values are to be $I_{CQ} = 1\text{ mA}$ and $V_{CEQ} = 6\text{ V}$




Solution

- Collector resistor $R_C = \frac{V_{CC} - V_{CEQ}}{I_{CQ}} = \frac{12 - 6}{1} = 6 \text{ k}\Omega$

- Base current $I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{1 \text{ mA}}{100} \Rightarrow 10 \mu\text{A}$

- Base resistor $R_B = \frac{V_{CC} - V_{BE(\text{on})}}{I_{BQ}} = \frac{12 - 0.7}{10 \mu\text{A}} = 1.13 \text{ M}\Omega$

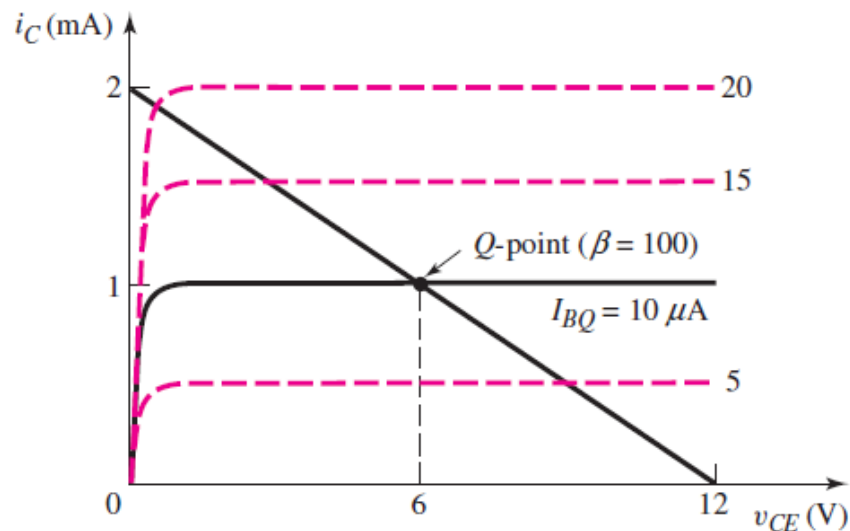- The transistor characteristics, load line, and Q-point for this set of conditions



Effect of β variation

- Assume
 - The resistor values are fixed
 - **The designed resistor values are available**
- The base current


$$I_{BQ} = \frac{V_{CC} - V_{BE(\text{on})}}{R_B} = \frac{12 - 0.7}{1.13 \text{ M}\Omega} = 10 \mu\text{A (unchanged)}$$

- Base current for this circuit configuration is independent of β
- Collector current $I_{CQ} = \beta I_{BQ}$
- The load line is fixed. However, the Q-point will change
- $V_{CEQ} = V_{CC} - I_{CQ} R_C$

β	50	100	150
Q-point values	$I_{CQ} = 0.50 \text{ mA}$ $V_{CEQ} = 9 \text{ V}$	$I_{CQ} = 1 \text{ mA}$ $V_{CEQ} = 6 \text{ V}$	$I_{CQ} = 1.5 \text{ mA}$ $V_{CEQ} = 3 \text{ V}$


Solution

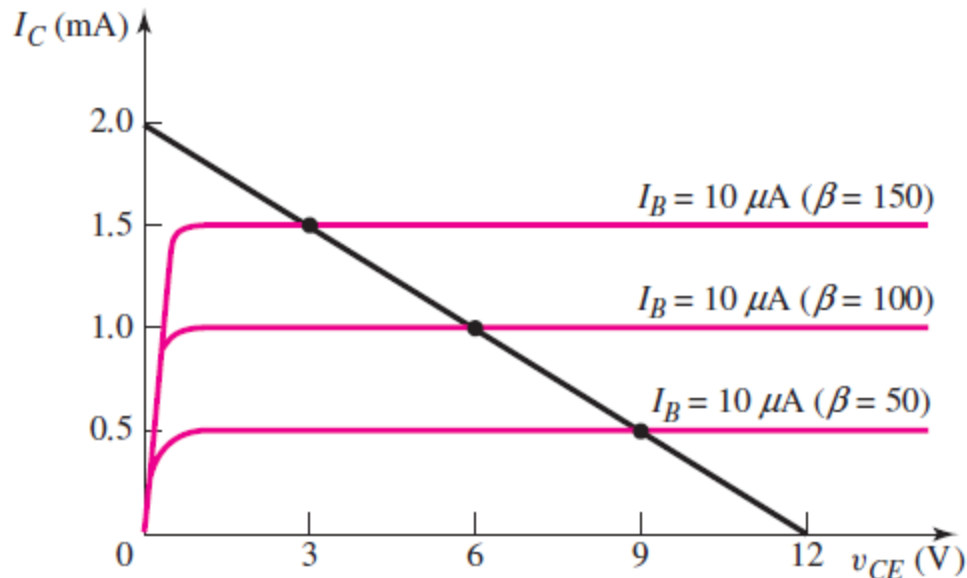- With a single base resistor, the Q-point is not stabilized against variations in β
- As β changes, the Q-point varies significantly
- Value of $1.13 \text{ M}\Omega$ for R_B will establish the required base current
- **This resistance is too large to be used in integrated circuits**



Voltage Divider Biasing and Bias Stability

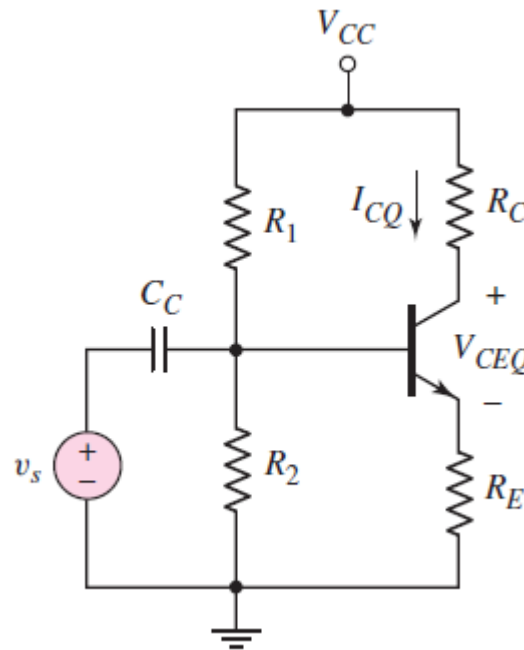- The single bias resistor R_B in single Base Resistor Biasing circuit is replaced by a pair of resistors R_1 and R_2 , and an emitter resistor R_E is added
- The ac signal is coupled to the base of the transistor through the coupling capacitor C_C (**acts as an open circuit to dc**)




DC circuit with a Thevenin equivalent base circuit

$$V_{TH} = [R_2/(R_1 + R_2)]V_{CC}$$

and the equivalent Thevenin resistance is

$$R_{TH} = R_1 \parallel R_2$$

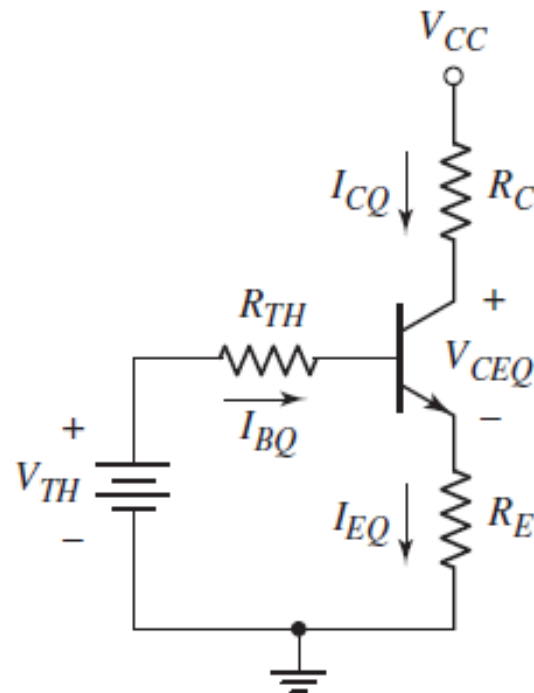

Thevenin's Equivalent Circuit

- Applying Kirchhoff's law around the B-E loop

$$V_{TH} = I_{BQ}R_{TH} + V_{BE(on)} + I_{EQ}R_E$$

- If the transistor is biased in the forward-active mode


$$I_{EQ} = (1 + \beta)I_{BQ}$$

$$I_{BQ} = \frac{V_{TH} - V_{BE(on)}}{R_{TH} + (1 + \beta)R_E}$$

$$I_{CQ} = \beta I_{BQ} = \frac{\beta(V_{TH} - V_{BE(on)})}{R_{TH} + (1 + \beta)R_E}$$

Design Example

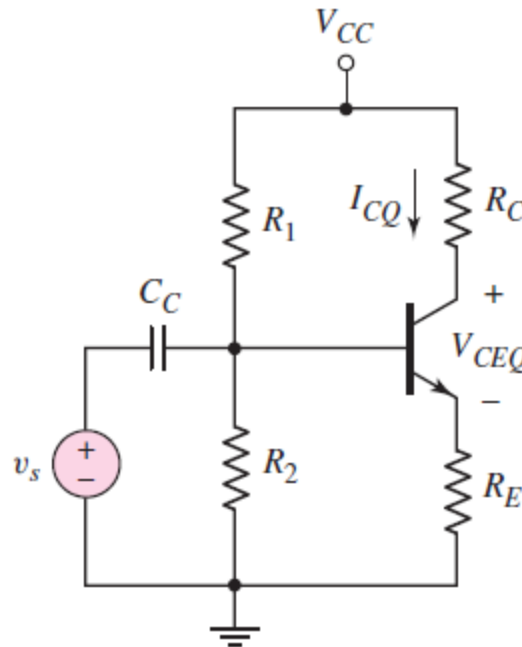- Let $R_1 = 56 \text{ k}$, $R_2 = 12.2 \text{ k}$, $R_C = 2 \text{ k}$, $R_E = 0.4 \text{ k}$, $V_{CC} = 10 \text{ V}$, $V_{BE(\text{on})} = 0.7 \text{ V}$, and $\beta = 100$
- Analyze a circuit and determine the **change in the Q-point** with a variation in β



Solution

$$R_{TH} = R_1 \parallel R_2 = 56 \parallel 12.2 = 10.0 \text{ k}\Omega$$

and

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) \cdot V_{CC} = \left(\frac{12.2}{56 + 12.2} \right) (10) = 1.79 \text{ V}$$

$$I_{BQ} = \frac{V_{TH} - V_{BE(\text{on})}}{R_{TH} + (1 + \beta)R_E} = \frac{1.79 - 0.7}{10 + (101)(0.4)} \Rightarrow 21.6 \mu\text{A}$$

The collector current is

$$I_{CQ} = \beta I_{BQ} = (100)(21.6 \mu\text{A}) \Rightarrow 2.16 \text{ mA}$$

and the emitter current is

$$I_{EQ} = (1 + \beta)I_{BQ} = (101)(21.6 \mu\text{A}) \Rightarrow 2.18 \text{ mA}$$

The quiescent C–E voltage is then


$$V_{CEQ} = V_{CC} - I_{CQ}R_C - I_{EQ}R_E = 10 - (2.16)(2) - (2.18)(0.4) = 4.81 \text{ V}$$

- These results show that the transistor is biased in the active region

Analysis

β	50	100	150
Q -point values	$I_{BQ} = 35.9 \mu\text{A}$ $I_{CQ} = 1.80 \text{ mA}$ $V_{CEQ} = 5.67 \text{ V}$	$I_{BQ} = 21.6 \mu\text{A}$ $I_{CQ} = 2.16 \text{ mA}$ $V_{CEQ} = 4.81 \text{ V}$	$I_{BQ} = 15.5 \mu\text{A}$ $I_{CQ} = 2.32 \text{ mA}$ $V_{CEQ} = 4.40 \text{ V}$

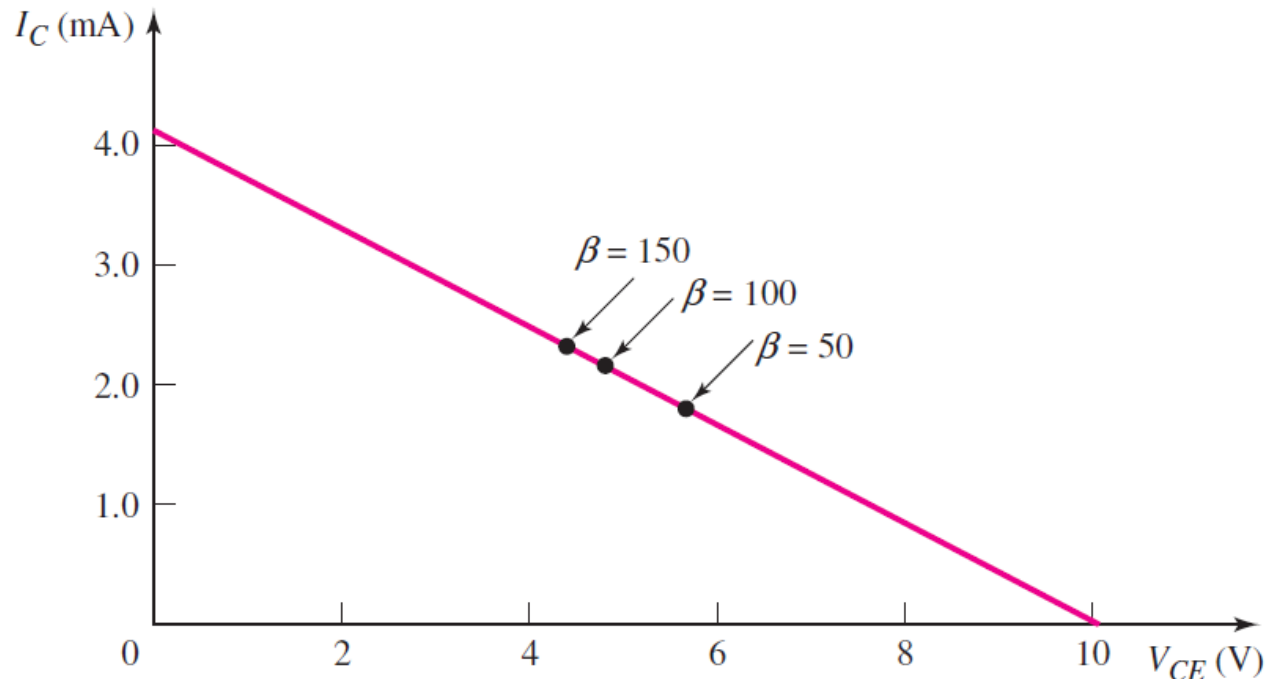For a **3 : 1** ratio in β ,
the collector current
and collector–
emitter voltage
change by only a
1.29 : 1 ratio



Analysis & Comparison

- The voltage divider circuit of R_1 and R_2 can bias the transistor in its active region using resistor values in **low kilo Ohm** range
- In contrast, single resistor biasing requires a resistor in the **mega ohm range**
- The change in I_{CQ} and V_{CEQ} with a change in β has been substantially reduced compared to the change in the single resistor biasing circuit
- Including an emitter resistor R_E
 - Helps to stabilize the Q-point with respect to variations in β
 - Introduces negative feedback,
 - Negative feedback tends to stabilize circuits

Comments

- Considering the equation

$$I_{CQ} = \beta I_{BQ} = \frac{\beta(V_{TH} - V_{BE(on)})}{R_{TH} + (1 + \beta)R_E}$$

- The design requirement for bias stability is $R_{TH} \ll (1 + \beta)R_E$.
- Consequently, the collector current is approximately

$$I_{CQ} \cong \frac{\beta(V_{TH} - V_{BE(on)})}{(1 + \beta)R_E}$$

- Normally, $\beta \gg 1$; therefore, $\beta / (1 + \beta) \approx 1$, and

$$I_{CQ} \cong \frac{(V_{TH} - V_{BE(on)})}{R_E}$$


- Now the quiescent collector current is essentially a function of only the dc voltages and the emitter resistance
- Q-point is stabilized against β variations

Comments

- However, if R_{TH} is too small, then R_1 and R_2 are small, and excessive power is dissipated in these resistors
- The general rule is that a circuit is considered **bias stable** when

$$R_{TH} \cong 0.1(1 + \beta)R_E$$

Design Example

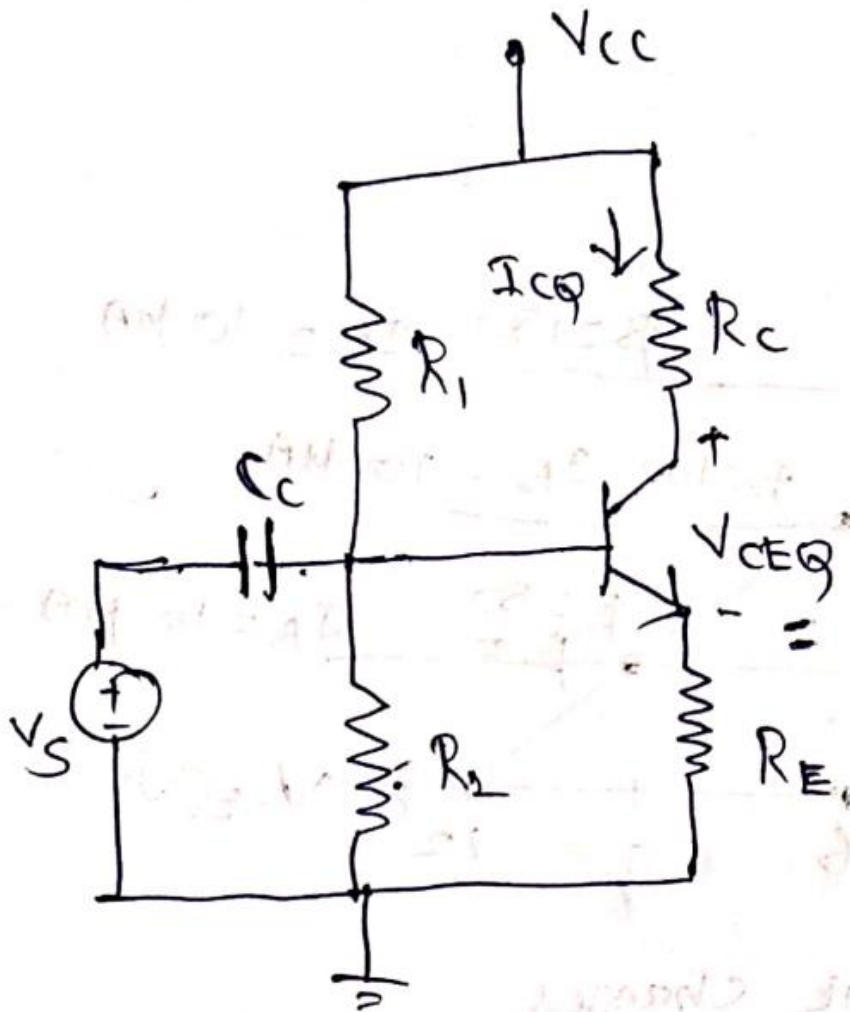

$$V_{CC} = 5 \text{ V}$$

$$R_C = 1 \text{ k}\Omega$$

choose R_E & determine
bias resistors R_1 & R_2

Such that the circuit is
considered bias stable
and that $V_{CEQ} = 3 \text{ V}$

Solution

$$\text{Let } \beta = 120 \quad V_{BE(Qn)} = 0.7 \text{ V}$$

$$I_{CQ} \approx I_{EQ}$$

$$\text{Let } R_E = 0.51 \text{ k}\Omega \quad (\text{standard value})$$

$$I_{CQ} = \frac{V_{CC} - V_{CEQ}}{R_C + R_E} = \frac{5 - 3}{1 + 0.51} = 1.32 \text{ mA}$$

$$V_{RE} = I_{EQ} \cdot R_E = 1.32 \text{ mA} \times 0.51 \text{ k}\Omega$$

$$= 0.673 \text{ V}$$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{1.32 \text{ mA}}{120} = 11 \text{ }\mu\text{A}$$

B) Thevenins Eqvt CLK

$$I_{BQ} = \frac{V_{Th} - V_{BE(on)}}{R_{Th} + (1 + \beta) R_E}$$

for bias stable circuit $\cdot R_{Th} = 0.1(1 + \beta) R_E$
 $= 6.17 \text{ k}\Omega$

$$I_{BQ} = \frac{V_{Th} - 0.7}{6.17 + 121 \times 0.51}$$

$$V_{Th} = 1.45 \text{ V}$$

$$V_{th} = V_{cc} \left(\frac{R_2}{R_1 + R_2} \right) = 5 \left(\frac{R_2}{R_1 + R_2} \right)$$

$$\frac{R_2}{R_1 + R_2} = 0.29$$

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} = 6.17 \text{ k}$$

$$R_1 \left(\frac{R_2}{R_1 + R_2} \right) = 6.17 \text{ k}$$

$$R_1 = \frac{6.17 \text{ k}}{0.29} = 21.3 \text{ k}\Omega$$

$$R_2 = 8.69 \text{ k}\Omega$$

Standard resistor values

$$R_1 = 20 \text{ k}\Omega$$

$$R_2 = 8.2 \text{ k}\Omega$$

Effect on Q-point variation values with β variation

$$R_1 = 20 \text{ k}\Omega$$

$$R_2 = 8.2 \text{ k}\Omega$$

$$R_{TH} = R_1 \parallel R_2 = \underline{5.82 \text{ k}\Omega}$$

$$V_{TH} = V_{CC} \left(\frac{R_2}{R_1 + R_2} \right) = 5 \left(\frac{8.2}{20 + 8.2} \right)$$

$$V_{TH} = \underline{1.454 \text{ V}}$$

$$I_{BQ} = \frac{V_{TH} - V_{BE(on)}}{R_{TH} + (1 + \beta) R_E}$$

$$I_{CQ} = \beta I_{BQ}$$

$$V_{CEQ} = V_{CC} - I_{CQ} R_C - I_{EQ} R_E$$

$$= V_{CC} - I_{CQ} R_C - \frac{I_{CQ}}{\alpha} R_E$$

$$V_{CEQ} = V_{CC} - I_{CQ} \left(R_C + \left(\frac{\beta + 1}{\beta} \right) R_E \right)$$

Analysis

- Collector current changes by only –8.2 percent when β changes by a factor of 2 (from 120 to 60), and changes by only +3.0 percent when β changes by +50 percent (from 120 to 180)
- The Q-point is now considered to be stabilized against variations in β
- Voltage divider resistors R1 and R2 have reasonable values in the kilo ohm range

β	60	120	180
Q-point values	$I_{BQ} = 20.4 \mu\text{A}$ $I_{CQ} = 1.23 \text{ mA}$ $V_{CEQ} = 3.13 \text{ V}$	$I_{BQ} = 11.2 \mu\text{A}$ $I_{CQ} = 1.34 \text{ mA}$ $V_{CEQ} = 2.97 \text{ V}$	$I_{BQ} = 7.68 \mu\text{A}$ $I_{CQ} = 1.38 \text{ mA}$ $V_{CEQ} = 2.91 \text{ V}$

References

- Donald A Neamen, Microelectronics: Circuit Analysis and Design / Edition 4, 2010.